

Lab 1 PSpice Simulation: Author 2

Figure 1: CMOS Inverter circuit with square wave input of 5V @ $f = 300$ kHz

[illegible]

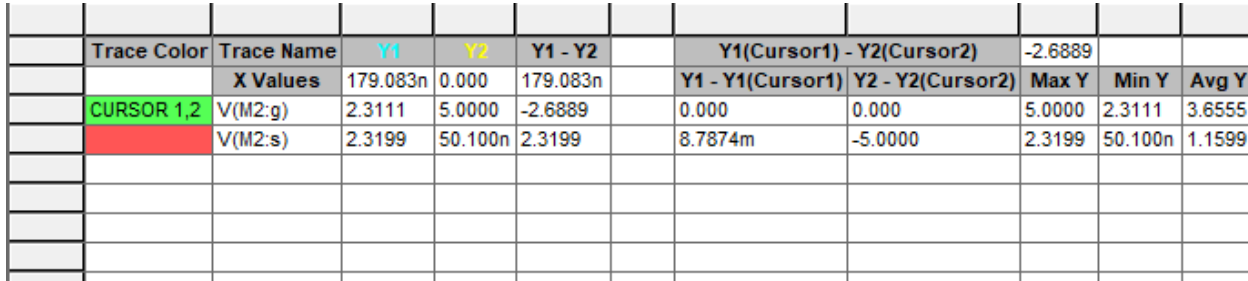
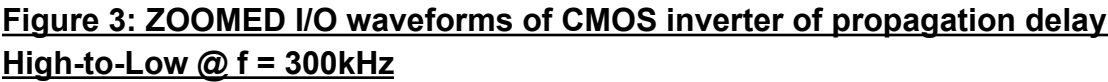
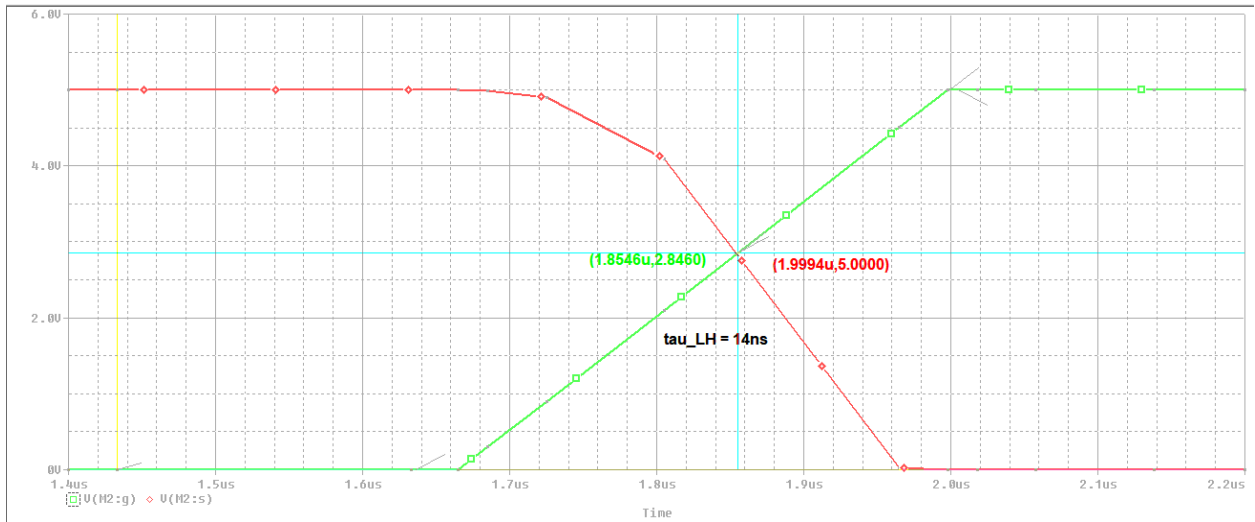


Figure 4: ZOOMED I/O waveforms of CMOS inverter of propagation delay
Low-to-High @ f = 300kHz

[illegible]

Case 4:

Figure 5: CMOS Inverter circuit with square wave input of 5V @ f = 900 kHz

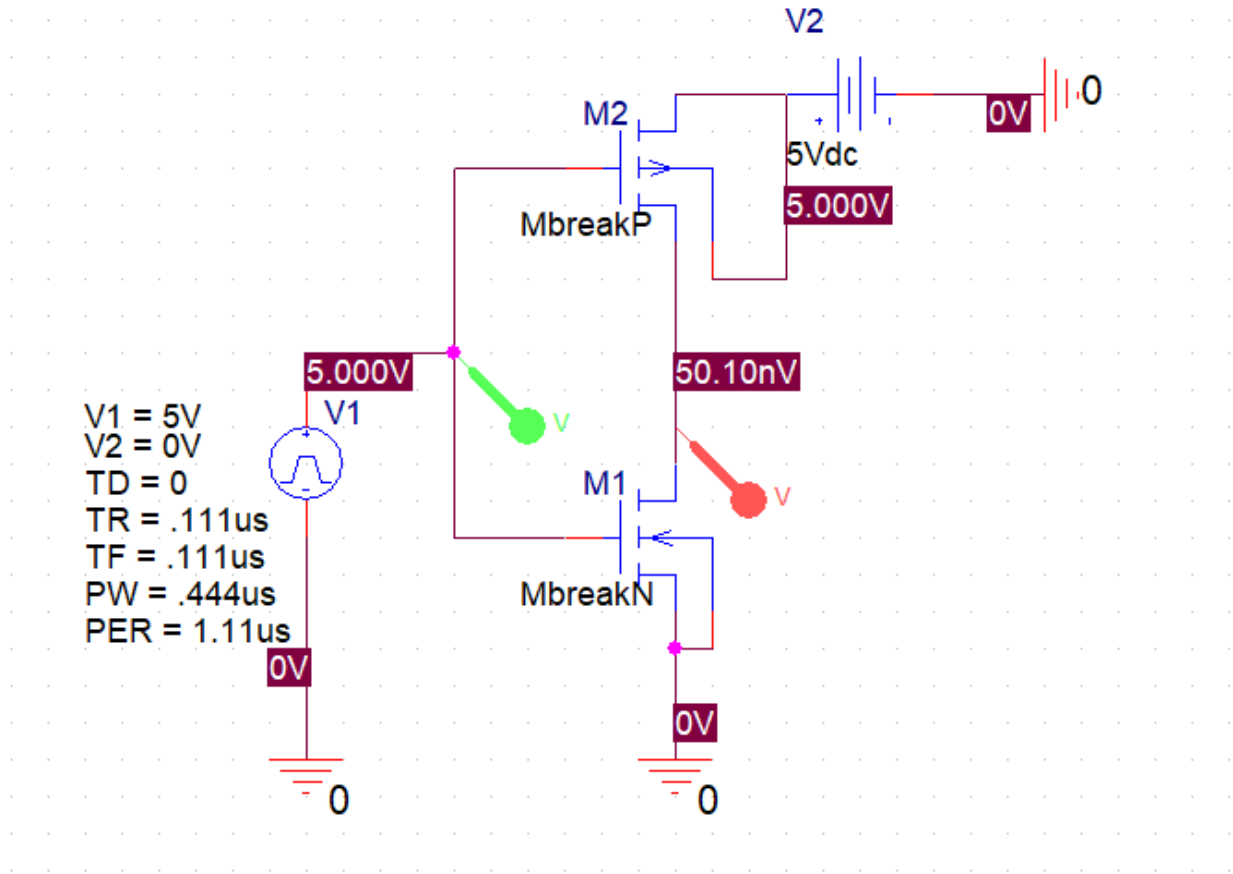


Figure 6: I/O waveforms of CMOS inverter with input of 5V @ f = 900kHz

	Trace Color	Trace Name	Y1	Y2	Y1 - Y2		Y1(Cursor1) - Y2(Cursor2)	0.000		
		X Values	1.7784u	0.000	1.7784u		Y1 - Y1(Cursor1) Y2 - Y2(Cursor2)	Max Y	Min Y	Avg Y
	CURSOR 1,2	V(M2:g)	5.0000	5.0000	0.000		0.000	0.000	5.0000	5.0000
		V(M2:s)	50.100n	90.595u	-90.544u		-5.0000	-4.9999	90.595u	50.100n
		V(M2:s)	50.100n	90.595u	-90.544u		-5.0000	-4.9999	90.595u	50.100n
		V1(V1)	5.0000	5.0000	0.000		0.000	0.000	5.0000	5.0000

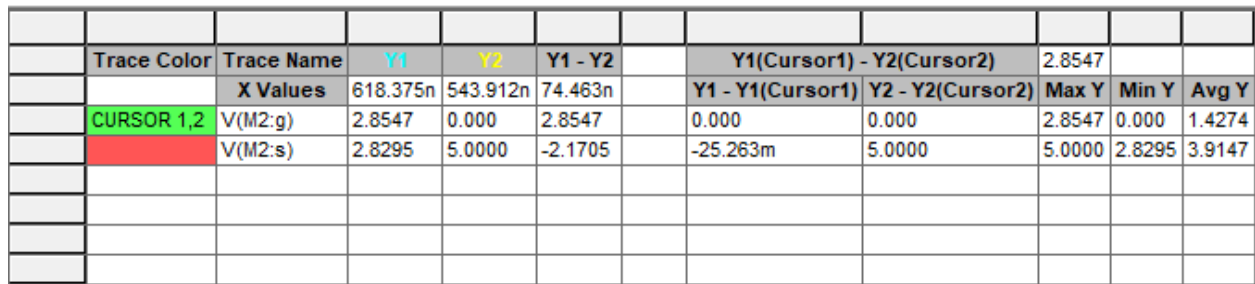


Figure 8: ZOOMED I/O waveforms of CMOS inverter of propagation delay
Low-to-High @ f = 900kHz

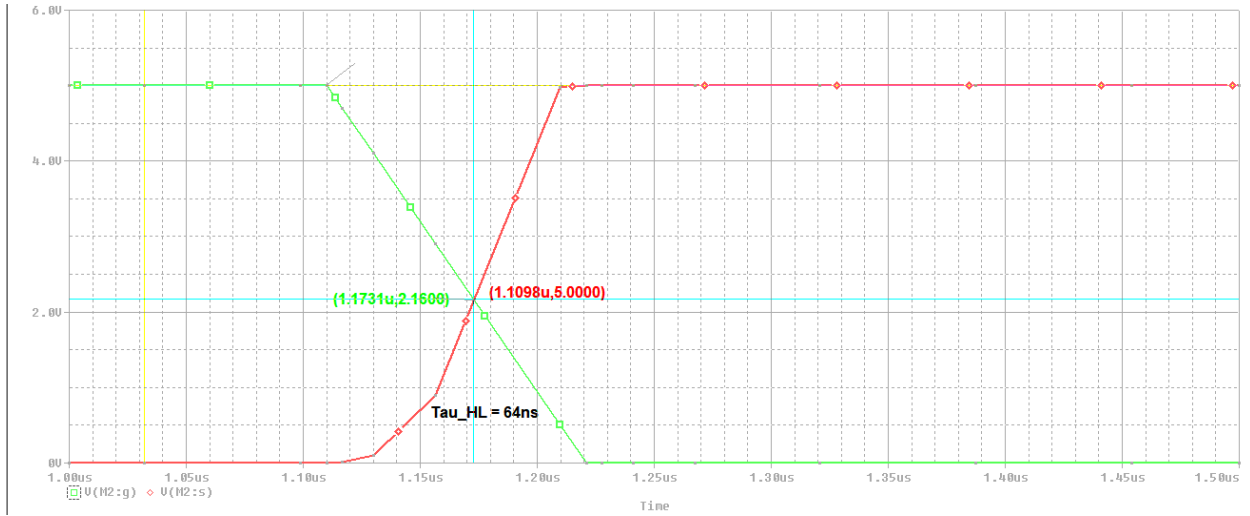
[illegible]

Figure 9: CMOS Inverter circuit with ramp wave input of 5V @ f = 200 kHz

[illegible]


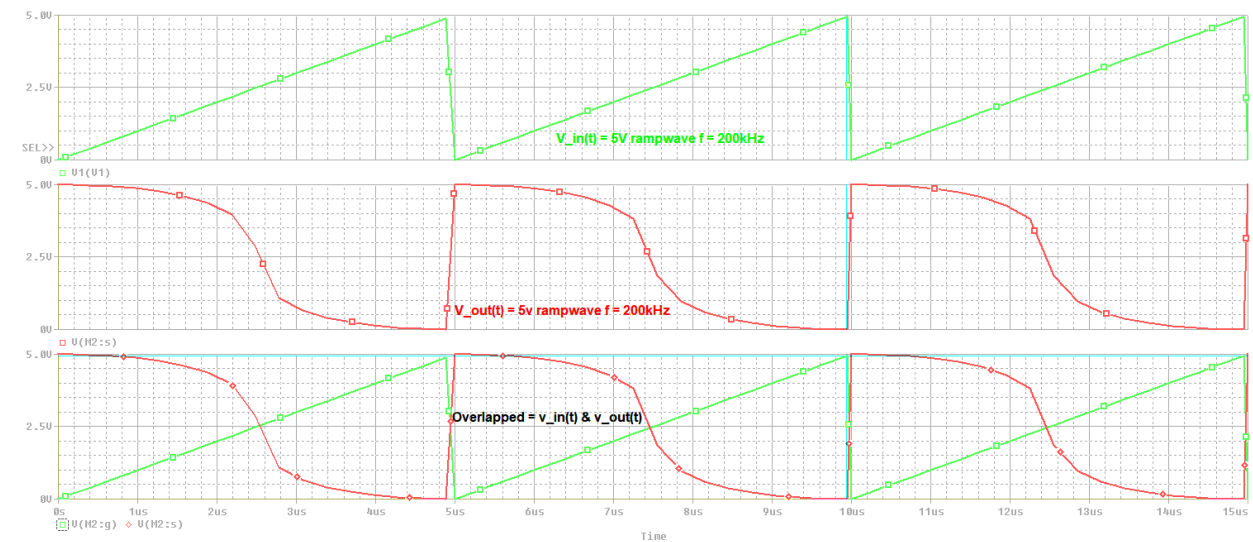
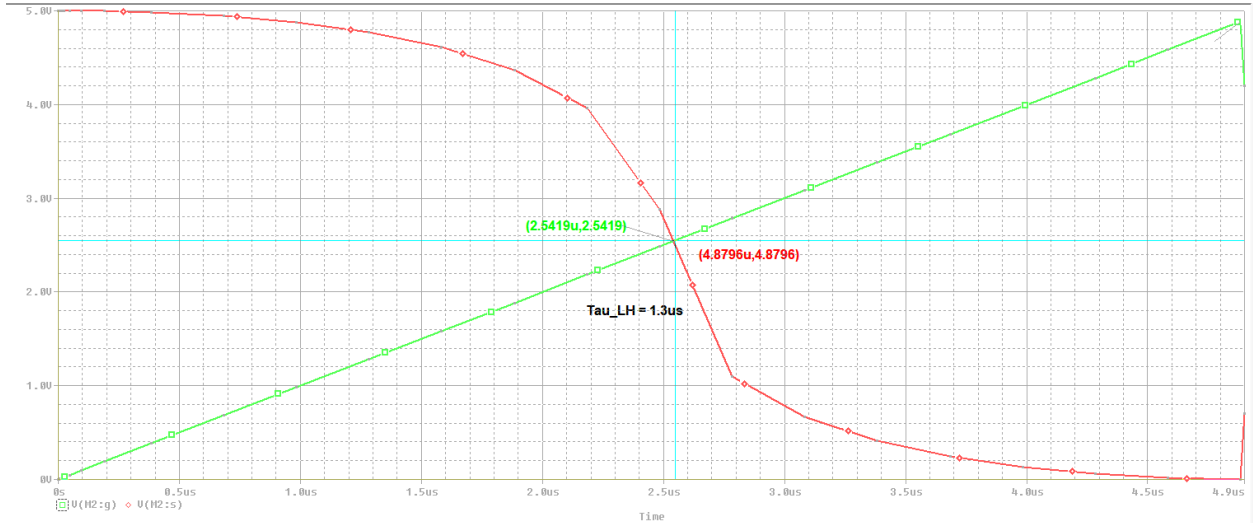


Figure 11: ZOOMED I/O waveforms of CMOS inverter of propagation delay
Low-to-High @ f = 200kHz

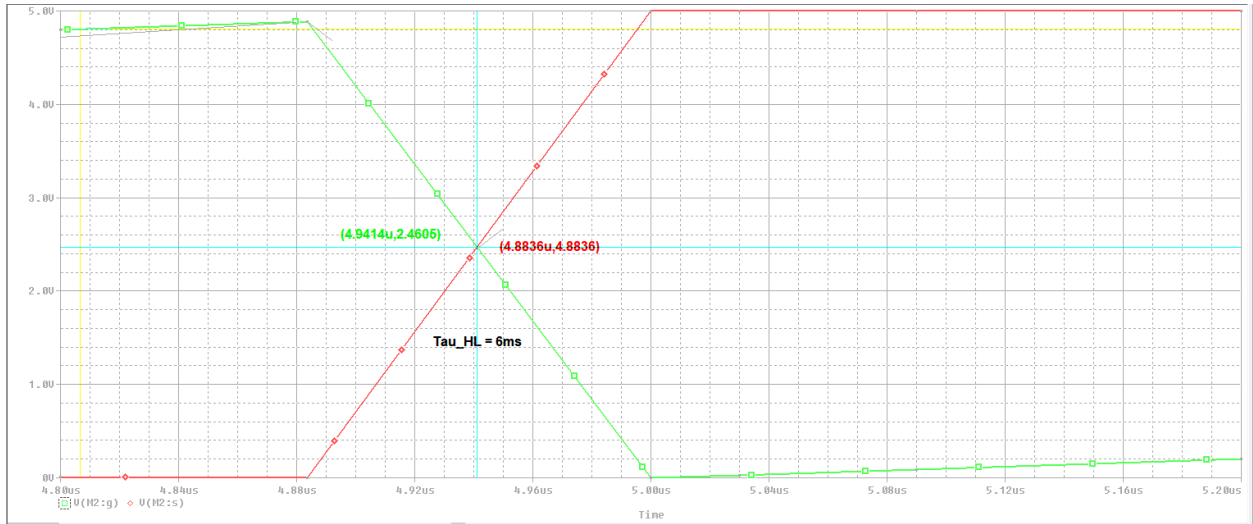

	Trace Color	Trace Name	Y1	Y2	Y1 - Y2	Y1(Cursor1) - Y2(Cursor2)	2.5487			
		X Values	2.5487u	0.000	2.5487u	Y1 - Y1(Cursor1)	Y2 - Y2(Cursor2)	Max Y	Min Y	Avg Y
	CURSOR 1,2	V(M2:g)	2.5487	0.000	2.5487	0.000	0.000	2.5487	0.000	1.2743
		V(M2:s)	2.4956	5.0000	-2.5044	-53.074m	5.0000	5.0000	2.4956	3.7478

Figure 12: ZOOMED I/O waveforms of CMOS inverter of propagation delay High-to-Low @ $f = 200\text{kHz}$

[illegible]